
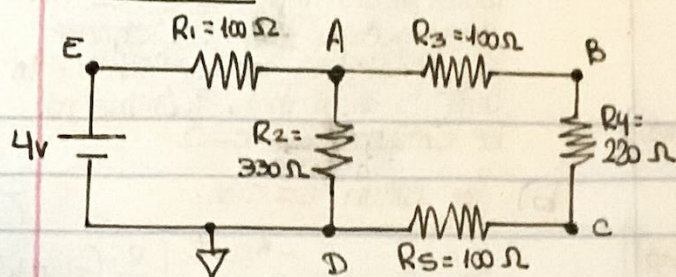


HOMEWORK 2:

QUESTION 01:

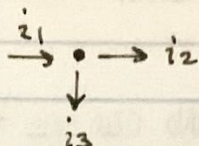

NODE A:



$$i_1 = i_2 + i_3$$


$$\frac{V_E - V_A}{100} = \frac{V_A - V_B}{100} + \frac{V_A - V_D}{330}$$

$$V_E - V_A = V_A - V_B + \frac{10}{33}(V_A - V_D)$$

$$4 - V_A = V_A - V_B + \frac{10}{33}V_A$$

$$\frac{76}{33}V_A - V_B = 4$$

NODE B:

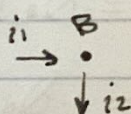

$$i_1 = i_2$$


$$\frac{V_A - V_B}{100} = \frac{V_B - V_C}{220}$$

$$V_A - V_B = \frac{5}{11}(V_B - V_C)$$

$$V_A - V_B = \frac{5}{11}V_B - \frac{5}{11}V_C$$

$$V_A - \frac{16}{11}V_B + \frac{5}{11}V_C = 0$$

NODE C:

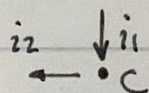

$$i_1 = i_2$$

$$\frac{V_B - V_C}{220} = \frac{V_C - V_D}{100}$$

$$V_B - V_C = \frac{11}{5}(V_C - V_D)$$

$$V_B - \frac{16}{5}V_C = 0$$

Summarizing:



$$\begin{pmatrix} 76/33 & -1 & 0 \\ 1 & -16/11 & 5/11 \\ 0 & 1 & -16/5 \end{pmatrix} \begin{pmatrix} V_A \\ V_B \\ V_C \end{pmatrix} = \begin{pmatrix} 4 \\ 0 \\ 0 \end{pmatrix}$$

A. $\rightarrow \begin{pmatrix} V_A \\ V_B \\ V_C \end{pmatrix} = \begin{pmatrix} 231/89 \\ 176/89 \\ 55/89 \end{pmatrix} = \begin{pmatrix} 2.6 \\ 1.98 \\ 0.62 \end{pmatrix} \text{ V}$


B. $\bullet I_{R1} = \frac{V_E - V_A}{100} = \frac{4 - 2.6}{100} = 14 \text{ mA}$ $\left| \begin{array}{l} V_E = 4V \\ V_D = 0V \end{array} \right.$

$\bullet I_{R2} = \frac{V_A - V_D}{330} = \frac{2.6}{330} = 7.88 \text{ mA}$

$\bullet I_{R3} = I_{R4} = I_{R5} = \frac{V_A - V_B}{100} = \frac{2.6 - 1.98}{100} = 6.2 \text{ mA}$

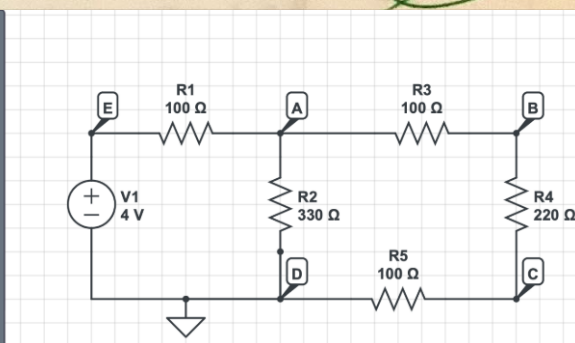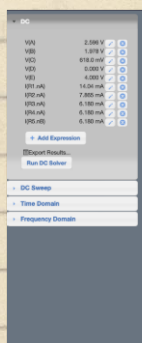

QUESTION 02:

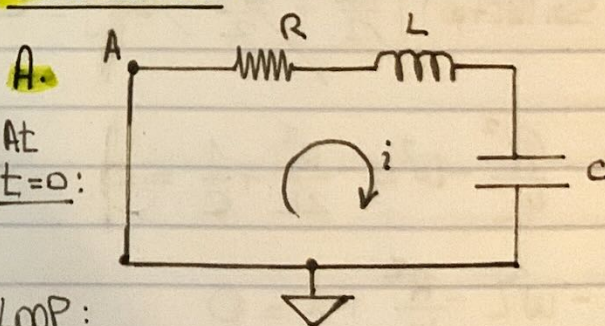

At $t=0$:

LOOP:

$$V_A - R i - L \frac{di}{dt} - \frac{q}{C} = 0$$

$$R i + L \frac{di}{dt} + \frac{q}{C} = 0 \quad \text{but } i = \frac{dq}{dt}$$

$$L \frac{d^2 q}{dt^2} + R \frac{dq}{dt} + \frac{q}{C} = 0$$

- $L \frac{d^2 q}{dt^2} \rightarrow$ Voltage drop across the inductor due to the self-induced emf.
- $R \frac{dq}{dt} \rightarrow$ Voltage drop due to the resistance R.
- $q/C \rightarrow$ Voltage drop due to the accumulation of charge in the capacitor.

B. $q(t) = Q_0 e^{-\frac{R}{2L}t} \cos(\omega t + \phi)$

$$\frac{dq(t)}{dt} = -\frac{Q_0 R}{2L} e^{-\frac{R}{2L}t} \cos(\omega t + \phi) - Q_0 \omega e^{-\frac{R}{2L}t} \sin(\omega t + \phi)$$

$$= -Q_0 e^{-\frac{R}{2L}t} \left[\frac{R}{2L} \cos(\omega t + \phi) + \omega \sin(\omega t + \phi) \right]$$

$$\frac{d^2 q(t)}{dt^2} = \frac{Q_0 R}{2L} e^{-\frac{R}{2L}t} \left[\frac{R}{2L} \cos(\omega t + \phi) + \omega \sin(\omega t + \phi) \right] - Q_0 e^{-\frac{R}{2L}t} \left[-\frac{R\omega}{2L} \sin(\omega t + \phi) + \omega^2 \cos(\omega t + \phi) \right]$$

$$\rightarrow L \frac{d^2 q}{dt^2} + R \frac{dq}{dt} + \frac{q}{C} = 0$$

$$= \frac{Q_0 R}{2L} e^{-\frac{R}{2L}t} \left[\frac{R}{2L} \cos(\omega t + \phi) + \omega \sin(\omega t + \phi) \right] - Q_0 e^{-\frac{R}{2L}t} \left[-\frac{R\omega}{2L} \sin(\omega t + \phi) + \omega^2 \cos(\omega t + \phi) \right] - \frac{Q_0 R^2}{2L} e^{-\frac{R}{2L}t} \cos(\omega t + \phi) + Q_0 R e^{-\frac{R}{2L}t} \sin(\omega t + \phi) + \frac{Q_0}{C} e^{-\frac{R}{2L}t} \cos(\omega t + \phi) = 0$$

$$= \cos(\omega t + \phi) \left[\frac{R^2}{4L} - \omega^2 L - \frac{R^2}{2L} + \frac{1}{C} \right] + \sin(\omega t + \phi) \left[\frac{R\omega}{2} + \frac{R\omega}{2} - R\omega \right] = 0$$

$$\rightarrow \frac{R^2}{4L} - \omega^2 L - \frac{R^2}{2L} + \frac{1}{C} = 0$$

$$-\omega^2 L - \frac{R^2}{4L} + \frac{1}{C} = 0$$

$$\omega^2 L = \frac{1}{C} - \frac{R^2}{4L}$$

$$\omega^2 = \frac{1}{LC} - \frac{R^2}{4L^2}$$

$$\omega = \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$$

$q(t) = Q_0 e^{-R/2L t} \cos(\omega t + \phi)$ is solution if and only if $\omega = \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$

C.

a) Because at $t=0 \rightarrow q(0) \neq 0$, which means that $q/C \neq 0$. As a consequence, there is charge accumulated on the capacitor. In order to allow this, $q(t)$ has to be continuous at $t=0$.

b) the current equation:

$$i(t) = -\frac{dq(t)}{dt} = -Q_0 e^{-R/2L t} \left[\frac{R}{2L} \cos(\omega t + \phi) + \omega \sin(\omega t + \phi) \right]$$

We can see that the phase constant ϕ allows the system to have an initial charge $q(0)$ and current $i(0)$ as expected in an underdamped circuit. It has to be continuous because then $\frac{dq}{dt} = i$ and $\frac{d^2 q}{dt^2} = \frac{di}{dt}$ can be also continuous and the equation still working.

c) $q(0) = Q_0 \cos \phi$

d) $i(0) = -Q_0 \left[\frac{R}{2L} \cos \phi + \omega \sin \phi \right]$

Question 03

