

PHYS 222 - HOMEWORK 01:

Problem 01:

a) Let's consider the first row in the table:

$$\bullet \text{ Diameter} = 0.0201 \text{ inch} \left(\frac{0.0254 \text{ m}}{1 \text{ inch}} \right)$$

$$= 5.1054 \times 10^{-4} \text{ m}$$

$$\bullet \text{ We know that } \rightarrow R = \frac{\rho L}{A}$$

$$R = \frac{(1.724 \times 10^{-8} \Omega \cdot \text{m}) L}{\frac{\pi (5.1054 \times 10^{-4} \text{ m})^2}{4}} = 0.0842 \frac{\Omega}{\text{m}}$$

$$\frac{R}{L} = 0.0842 \frac{\Omega}{\text{m}}$$

As we can see, the resistance per unit length is $0.0842 \Omega/\text{m}$. Assuming a sample length of 1000 m (or 1000 ft with the right units) then we set the value in the table:

$$R(L=1000 \text{ m}) = 84.2 \Omega$$

This is just an indicator of the resistance of the AWG 24 wire per 1000 m, and is used as a reference to determine the resistance of longer/shorter wires of this type easily, like considering a 'density of resistance' or simply resistance per unit length.

b) For the AWG-26 $\rightarrow R = 40.81 \frac{\Omega}{1000 \text{ ft}}$

$$R(4 \text{ inch}) = 4 \text{ inch} \left(\frac{1 \text{ ft}}{12 \text{ inch}} \right) \left(\frac{40.81 \Omega}{1000 \text{ ft}} \right)$$

$$= 0.0136 \Omega = 13.6 \text{ m}\Omega$$


c) For N AWG-26 jumpers connected in series:

$$R = \sum_{i=1}^N R_{i \text{ AWG}} = 1 \Omega$$

$$= N R_{\text{AWG}} = N (0.0136) = 1 \Omega$$

$$N = 74 \text{ AWG jumpers.}$$

Problem 02:

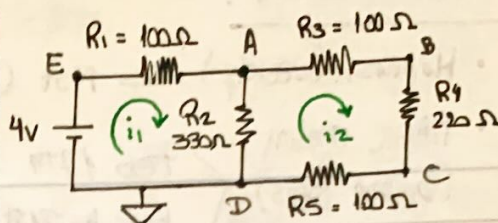

$$\bullet \text{ MESH 1: } 4 - 100i_1 - 330i_1 + 330i_2 = 0$$

$$430i_1 - 330i_2 = 4$$

$$\bullet \text{ MESH 2: } -100i_2 - 220i_2 - 330i_2 + 330i_1 = 0$$

$$330i_1 - 750i_2 = 0$$

$$\rightarrow \begin{pmatrix} 430 & -330 \\ 330 & -750 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \end{pmatrix} = \begin{pmatrix} 4 \\ 0 \end{pmatrix}$$

$$\begin{pmatrix} i_1 \\ i_2 \end{pmatrix} = \begin{pmatrix} 14.04 \\ 6.18 \end{pmatrix} \text{ mA}$$

Node A: $i_1 \rightarrow A \rightarrow i_2$
 $i_1 = i_2 + i_A$
 $i_A = i_1 - i_2 = 7.86 \text{ mA}$

a) $I_{R1} = i_1 = 14.04 \text{ mA}$

$$I_{R2} = i_A = 7.86 \text{ mA}$$

$$I_{R3} = I_{R4} = I_{R5} = i_2 = 6.18 \text{ mA}$$

b) $\Delta V_{EG} = V_E - V_G^{\text{Ground}} = V_E = 4 \text{ V}$

$$\bullet \Delta V_{EA} = V_E - V_A = 4 - V_A = 100(14.04 \times 10^{-3})$$

$$V_A = 4 - 1.404 = 2.596 \text{ V}$$

$$\bullet V_D = 0 \text{ V (Ground)}$$

$$\bullet \Delta V_{AB} = V_A - V_B = 2.596 - V_B = 100(6.18 \times 10^{-3})$$

$$V_B = 2.596 - 0.618 = 1.978 \text{ V}$$

$$\bullet \Delta V_{BC} = V_B - V_C = 1.978 - V_C = 1220(6.18 \times 10^{-3})$$

$$V_C = 1.978 - 1.3596 = 0.62 \text{ V}$$

Summary

$$V_A = 2.596 \text{ V}, V_B = 1.978 \text{ V}$$

$$V_C = 0.62 \text{ V}, V_D = 0 \text{ V}$$

$$V_E = 4 \text{ V}$$

Problem 03:

DC

V(A)	2.596 V
V(B)	1.978 V
V(C)	618.0 mV
V(D)	0.000 V
V(E)	4.000 V
I(R1.nA)	14.04 mA
I(R2.nA)	7.865 mA
I(R3.nA)	6.180 mA
I(R4.nA)	6.180 mA
I(R5.nA)	6.180 mA

+ Add Expression


Export Results...

Run DC Solver

DC Sweep

Time Domain

Frequency Domain

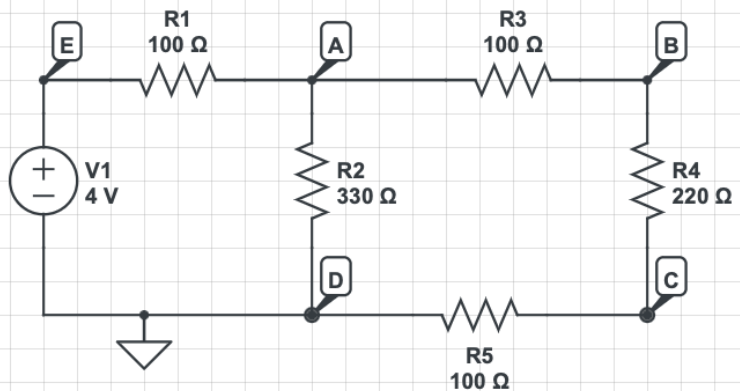

Problem 04:

a) Area of the plate:

$$A = (8.5 \text{ in})(11 \text{ in}) \left(\frac{2.54 \text{ cm}}{1 \text{ in}} \right)^2$$

$$= 0.0603 \text{ m}^2$$

Assuming the thickness d of a piece of paper as $\rightarrow d = 10^{-3} \text{ m}$

$$C = \frac{\epsilon_0 A}{d}$$

$$= \frac{(8.85 \times 10^{-12} \text{ F} \cdot \text{m}^{-1})(0.0603 \text{ m}^2)}{10^{-3} \text{ m}}$$

$$= 5.34 \times 10^{-10} \text{ F}$$

$$= 0.534 \text{ nF}$$

b) We know that $\tau = RC$

$$R = \frac{\tau}{C} = \frac{10^{-3} \text{ s}}{0.534 \times 10^{-9} \text{ F}}$$

$$= 1.87 \times 10^6 \Omega$$